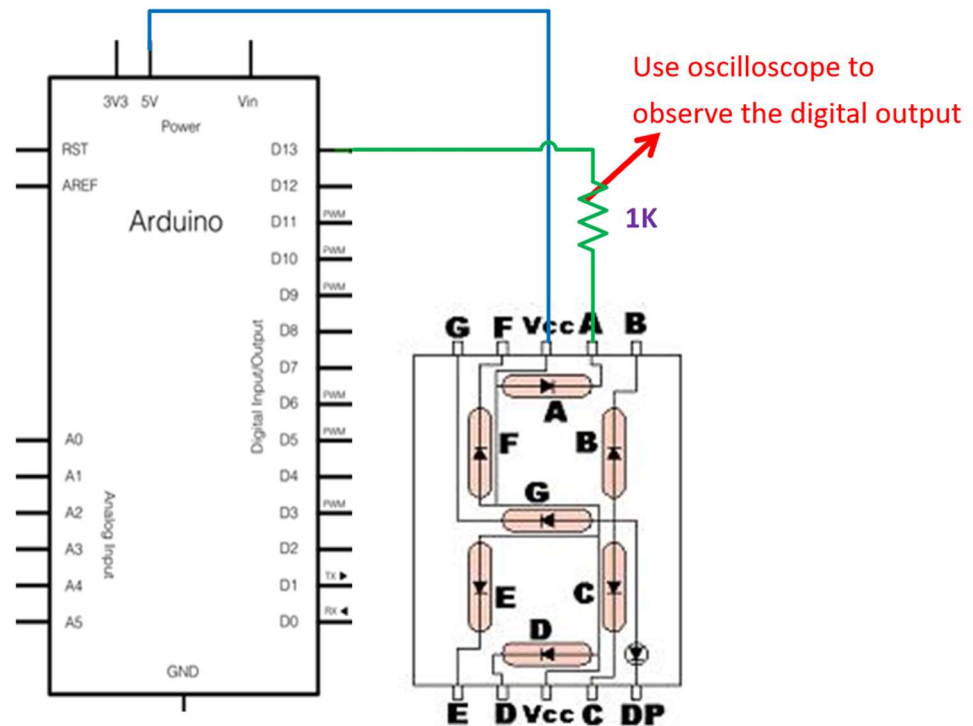


REPORT

Experiment 1: LED Blink.




NOTE: use DC coupling to observe the waveforms, and use cursor/measure to mark V_{high} and V_{low} .

What is a seven-segment display?

Basically, they are 7(line segments) + 1(dot) LEDs with a commonly connected end. There are 2 types of 7-segment display, common cathode, and common anode.

[1]

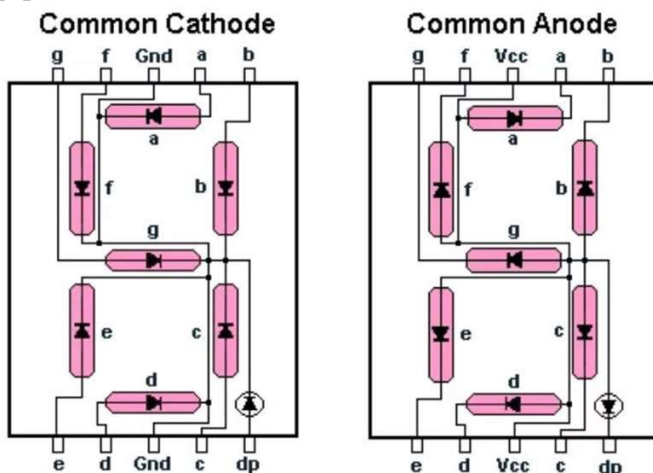


Common cathode:

The cathodes of LEDs are connected together, so if the input signal of an LED is **HIGH**, the corresponding LED would be turned on.

Common anode:

In contrast, the LED of the common anode type would be turned on if the input signal is **LOW**.

Circuit Analysis

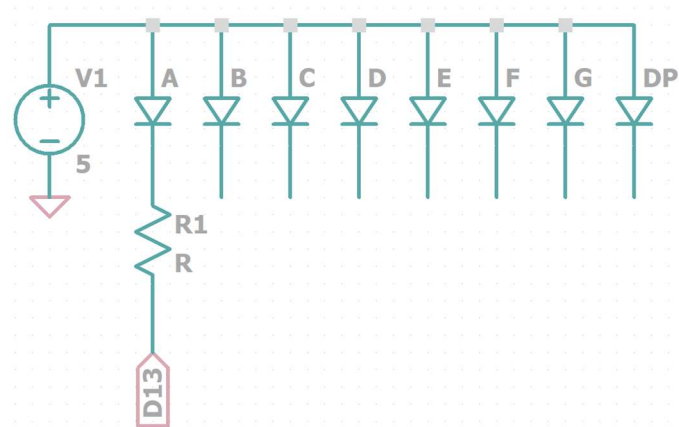


D13 is an input signal of the 7-segment display, if D13 is LOW(0V), the voltage drop of LED A would be 5V, and LED A would be turned on. On the contrary, if D13 is HIGH, the voltage drop of LED A would be 0V, LED A would be turned off.

D13	LED A
HIGH	Off
LOW	On

Simulation

0.5Hz

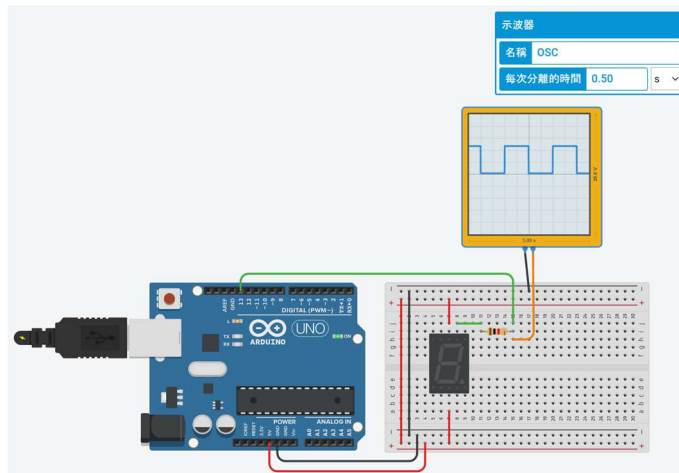


```

1  int led = 13;
2  int hT = 1000;
3
4  void setup()
5  {
6      pinMode(led, OUTPUT);
7  }
8
9  void loop()
10 {
11     digitalWrite(led, LOW);
12     delay(hT);
13     digitalWrite(led, HIGH);
14     delay(hT);
15 }

```


1Hz

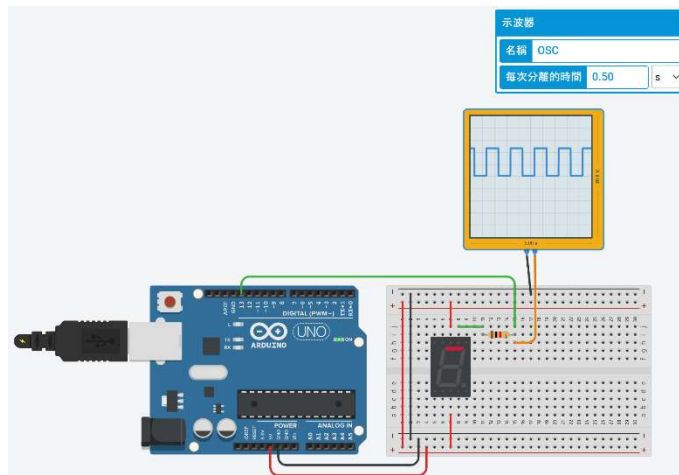

```

1  int led = 13;
2  int hT = 500;
3
4  void setup()
5  {
6      pinMode(led, OUTPUT);
7  }
8
9  void loop()
10 {
11     digitalWrite(led, LOW);
12     delay(hT);
13     digitalWrite(led, HIGH);
14     delay(hT);
15 }

```

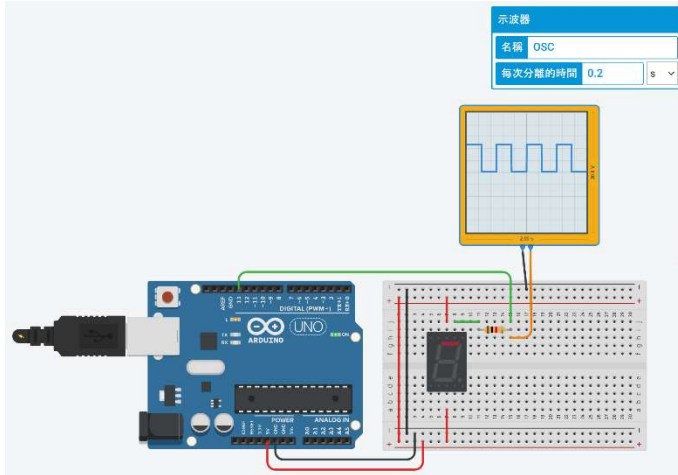

```


1  int led = 13;
2  int hT = 250;
3
4  void setup()
5  {
6      pinMode(led, OUTPUT);
7  }
8
9  void loop()
10 {
11     digitalWrite(led, LOW);
12     delay(hT);
13     digitalWrite(led, HIGH);
14     delay(hT);
15 }

```

Data

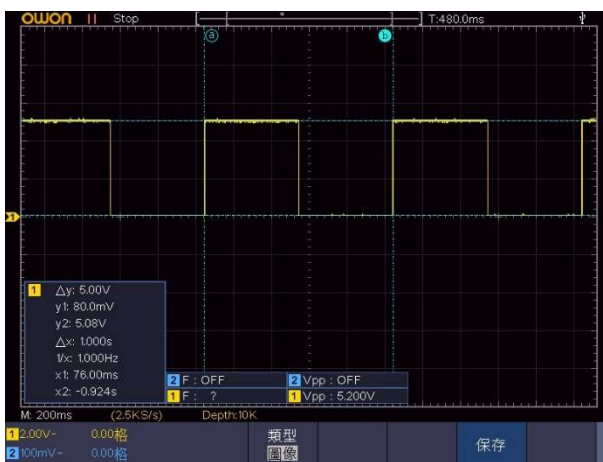
1.

Arduino D13 output waveform with frequency 1Hz.



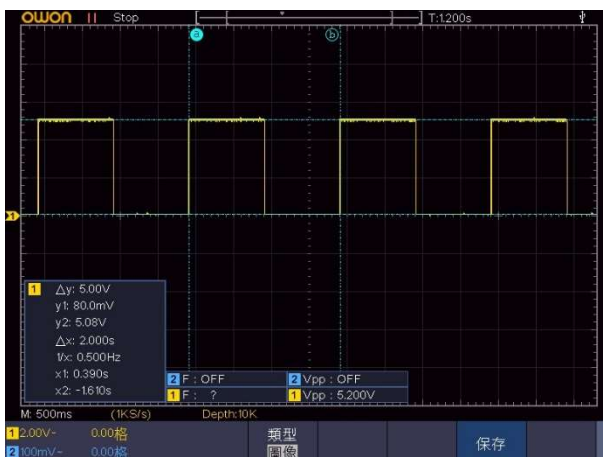
2.

Arduino D4 output waveform with frequency 0.5Hz.



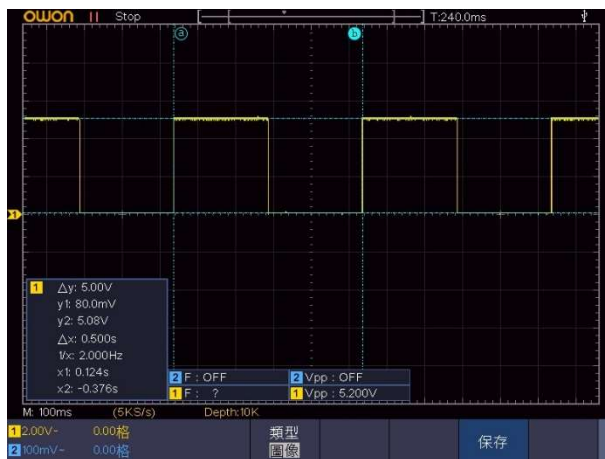3.

Arduino D4 output waveform with frequency 2Hz.



Question:

What output level (high/low) will make LED turn light or dark? Why?


LOW (0V). Because the 7-segment display we use is a common anode 7-segment display.

Demo

EXP1


<https://youtu.be/ottNDeb2jJo>

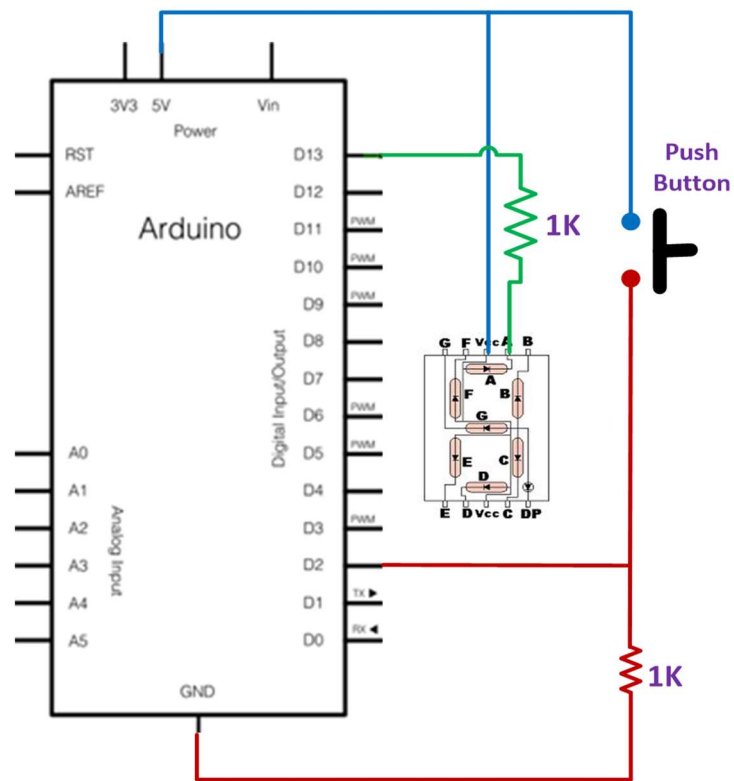Experiment 2: LED Blink with push button.




What is pull-high/pull-low circuit?

Pull-High

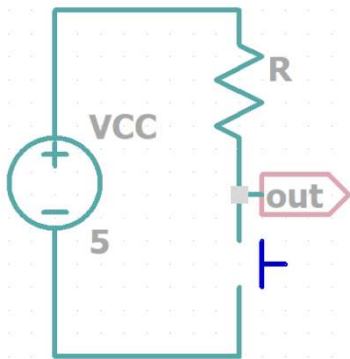


Pull-Low

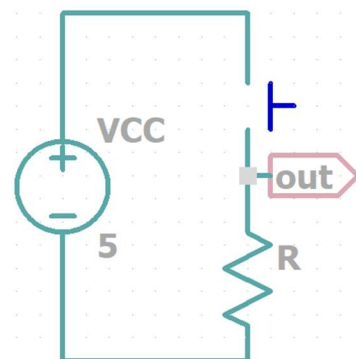


Button	Output
Release	HIGH
Press	LOW

Button	Output
Release	LOW
Press	HIGH

Circuit Analysis

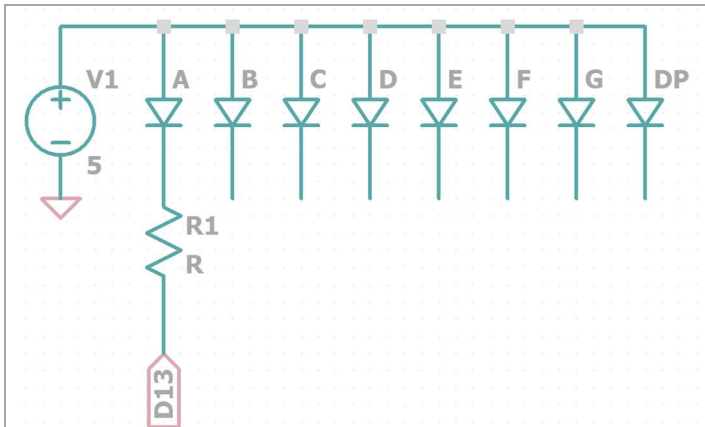


The same as the previous experiment.

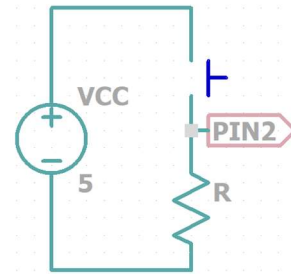

It's a pull-low circuit, and it's output would be the input signal of Arduino (connected to PIN2).

Simulation

Pull-Low

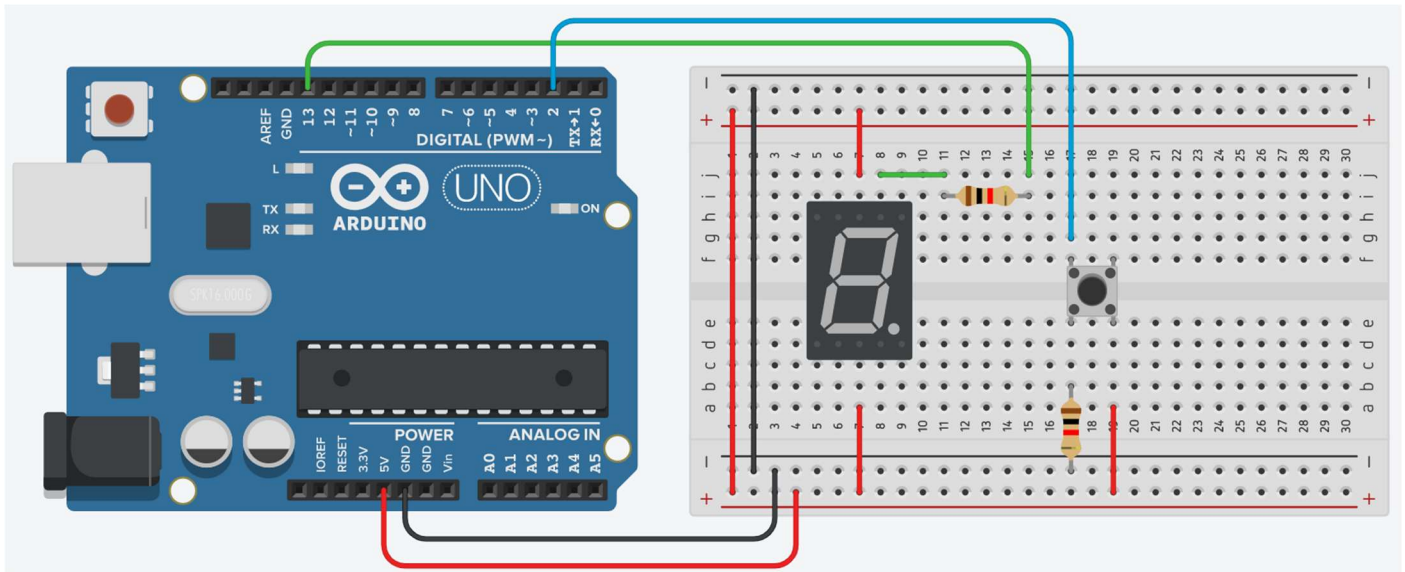

```
int pushButton = 8;
int led = 13;
void setup()
{
  // initialize serial communication at 9600 bits per second:
  Serial.begin(9600);


  pinMode(pushButton, INPUT);
  pinMode(led, OUTPUT);
}
```

```

void loop()
{
  // read the input pin:
  int buttonState = digitalRead(pushButton);
  if (buttonState == LOW)
  {
    digitalWrite(led, LOW);
    delay(1000);
    digitalWrite(led, HIGH);
    delay(1000);
    Serial.println(buttonState);
  }
  else
  {
    digitalWrite(led, LOW);
    Serial.println(buttonState);
  }
}

```

Pull-High

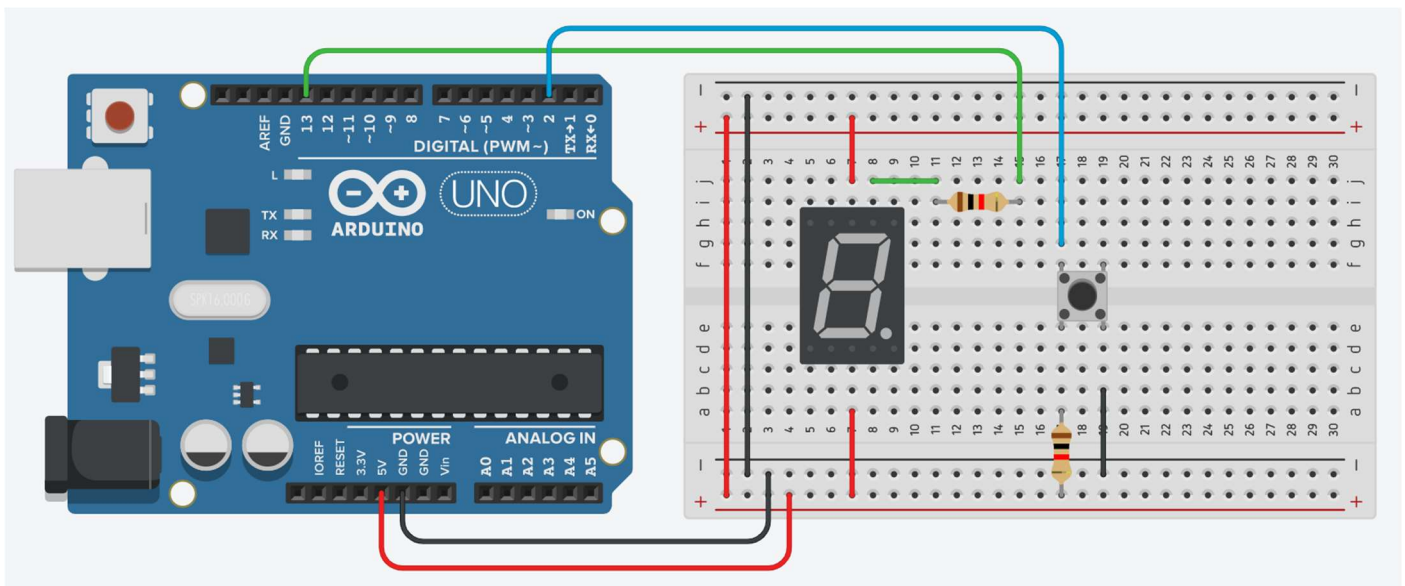

```

int pushButton = 8;
int led = 13;
void setup()
{
  Serial.begin(9600);
  pinMode(pushButton, INPUT);
  pinMode(led, OUTPUT);
}

```



```
void loop()
{
  int buttonState = digitalRead(pushButton);
  if (buttonState == HIGH)
  {
    digitalWrite(led, LOW);
    delay(1000);
    digitalWrite(led, HIGH);
    delay(1000);
    Serial.println(buttonState);
  }
  else
  {
    digitalWrite(led, LOW);
    Serial.println(buttonState);
  }
}
```


Data

1.
Is this circuit a pull-high or pull-low type? pull-low.

2.
Measure pin D2 voltage using voltage meter:

Behavior	DC Voltage (V)
Pushbutton pressed	5
Pushbutton released	0

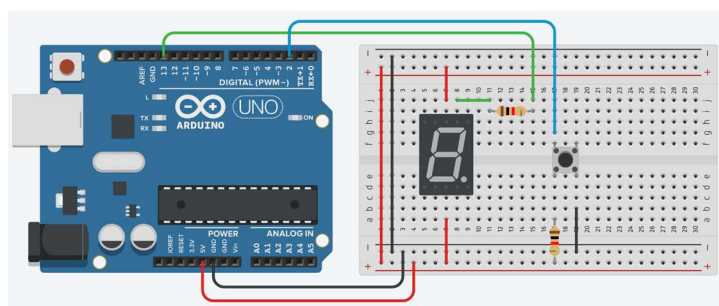3.
Change your circuit to another type and modify your circuit and sketch to achieve the same requirement.



Modified circuit:

Modified sketch:

```
int pushButton = 2;
int led = 13;
void setup()
{
  // initialize serial communication at 9600 bits per second:
  Serial.begin(9600);
  // make the pushbutton's pin an input and led's pin an output:
  pinMode(pushButton, INPUT);
  pinMode(led, OUTPUT);
}
void loop()
{
  // read the input pin:
  int buttonState = digitalRead(pushButton);

  // make LED blink and output buttonState.
  if (buttonState == HIGH)
  {
    digitalWrite(led, LOW); // turn the LED on (HIGH is the voltage level)
    delay(1000); // wait for a second
    digitalWrite(led, HIGH); // turn the LED off by making the voltage LOW
    delay(1000);
    Serial.println(buttonState);
  }
  else
  { // turn LED on and output buttonState.
    digitalWrite(led, LOW);
    Serial.println(buttonState);
  }
}
```

4.

Measure pin D2 voltage using voltage meter after step 3:

Behavior	DC Voltage (V)
Pushbutton pressed	0
Pushbutton released	5


5.
Attach your serial monitor screenshot
Release → Press

Pull - High	Pull-Low
<div><div>Serial Monitor ×</div><div>Message (Ctrl + Enter to send message to 'Arduino Uno' on 'COM3')</div><div>1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 0 0 0 0 0 0 0 0 0 0 0</div></div>	<div><div>Serial Monitor ×</div><div>Message (Ctrl + Enter to send message to 'Arduino Uno' on 'COM3')</div><div>- 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 1 1 1 1 1 1</div></div>

Demo

EXP2
<https://youtu.be/5OBm8n2hb1c>

Experiment 3: LED Marquee.

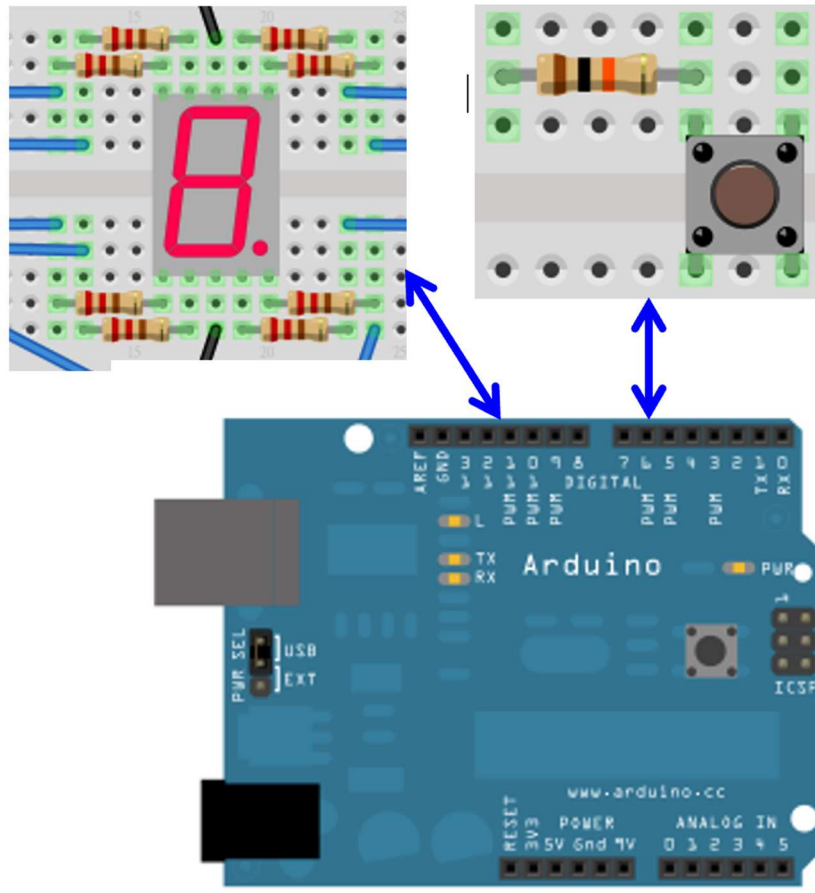

Attach your sketch and result pictures:

```
byte pinA=1, pinB=2, pinC=3, pinD=4, pinE=5, pinF=6, pinG=7, pinP=8;
byte pushButton = 13;
int buttonState;

void setup() {
  pinMode(pinA, OUTPUT); pinMode(pinB, OUTPUT); pinMode(pinC, OUTPUT);
  pinMode(pinD, OUTPUT); pinMode(pinE, OUTPUT); pinMode(pinF, OUTPUT);
  pinMode(pinG, OUTPUT); pinMode(pinP, OUTPUT);
  pinMode(pushButton, INPUT);
}

// show the specified LEDs of 7-segment
void showSevenSeg(byte A, byte B, byte C, byte D, byte E, byte F, byte G, byte P) {
  digitalWrite(pinA, A); digitalWrite(pinB, B); digitalWrite(pinC, C);
  digitalWrite(pinD, D); digitalWrite(pinE, E); digitalWrite(pinF, F);
  digitalWrite(pinG, G); digitalWrite(pinP, P);
}
```

```
void check()
{
  while(1)
  {
    buttonState = digitalRead(pushButton);
    if(!buttonState)
    {showSevenSeg(0,0,0,0,0,0,0);}
    else{break;}
  }
}


void loop() {
  showSevenSeg(0,1,1,1,1,1,1); // turn LED A of 7-segment on.
  delay(500);
  check();
  showSevenSeg(1,0,1,1,1,1,1); // turn LED A of 7-segment on.
  delay(500);
  check();
  showSevenSeg(1,1,0,1,1,1,1); // turn LED A of 7-segment on.
  delay(500);
  check();
  showSevenSeg(1,1,1,0,1,1,1); // turn LED A of 7-segment on.
  delay(500);
  check();
  showSevenSeg(1,1,1,1,0,1,1); // turn LED A of 7-segment on.
  delay(500);
  check();
}
```

Demo

EXP3

<https://youtu.be/cjjXVWf9tNQ>

Experiment 4: student ID Marquee.

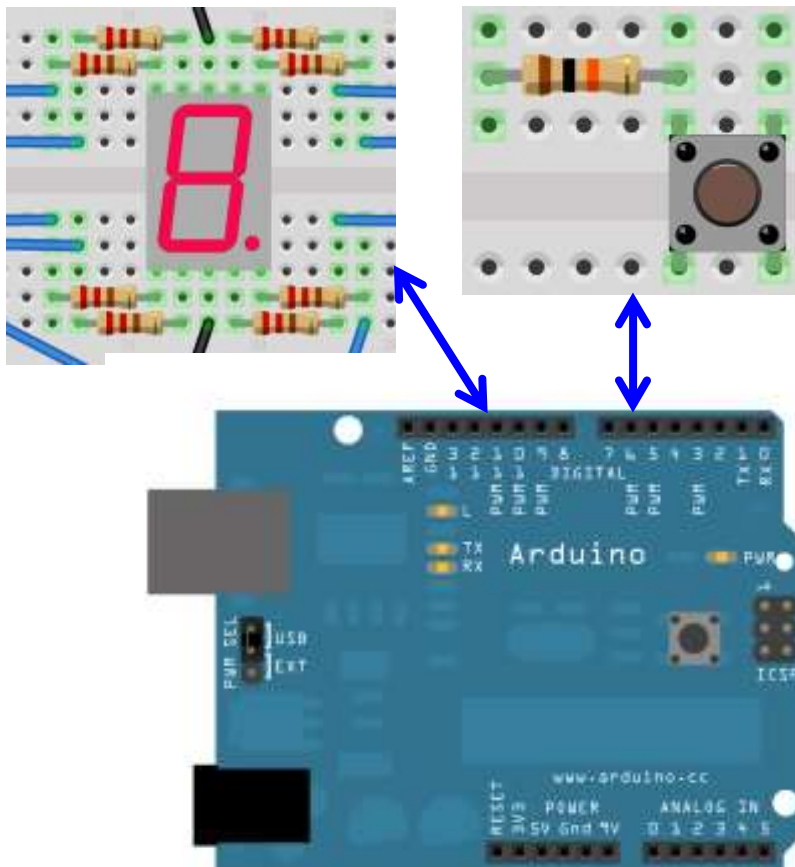

Attach your sketch and result pictures:

```
byte pinA=1, pinB=2, pinC=3, pinD=4, pinE=5, pinF=6, pinG=7, pinP=8;
byte pushButton = 13;
int buttonState;

void setup() {
  pinMode(pinA, OUTPUT); pinMode(pinB, OUTPUT); pinMode(pinC, OUTPUT);
  pinMode(pinD, OUTPUT); pinMode(pinE, OUTPUT); pinMode(pinF, OUTPUT);
  pinMode(pinG, OUTPUT); pinMode(pinP, OUTPUT);
  pinMode(pushButton, INPUT);
}

// show the specified LEDs of 7-segment
void showSevenSeg(byte A, byte B, byte C, byte D, byte E, byte F, byte G, byte P) {
  digitalWrite(pinA, A); digitalWrite(pinB, B); digitalWrite(pinC, C);
  digitalWrite(pinD, D); digitalWrite(pinE, E); digitalWrite(pinF, F);
  digitalWrite(pinG, G); digitalWrite(pinP, P);
}

void num(int n)
```

```
{
switch(n)
{
case 0:
    showSevenSeg(0,0,0,0,0,0,1,1);
    delay(500);
    break;
case 1:
    showSevenSeg(1,0,0,1,1,1,1,1);
    delay(500);
    break;
case 2:
    showSevenSeg(0,0,1,0,0,1,0,1);
    delay(500);
    break;
case 3:
    showSevenSeg(0,0,0,0,1,1,0,1);
    delay(500);
    break;
case 4:
    showSevenSeg(1,0,0,1,1,0,0,1);
    delay(500);
    break;
case 5:
    showSevenSeg(0,1,0,0,1,0,0,1);
    delay(500);
    break;
case 6:
    showSevenSeg(0,1,0,0,0,0,0,1);
    delay(500);
    break;
case 7:
    showSevenSeg(0,0,0,1,1,1,1,1);
    delay(500);
    break;
case 8:
    showSevenSeg(0,0,0,0,0,0,0,1);
    delay(500);
    break;
case 9:
    showSevenSeg(0,0,0,0,1,0,0,1);
```

```
    delay(500);
    break;
case 10:
    showSevenSeg(1,1,1,1,1,1,1);
    delay(200);
    break;
}
showSevenSeg(1,1,1,1,1,1,1);
delay(100);
}

void ID()
{
    int stuID[10]={10,1,0,9,5,1,1,2,0,8};
    for (int i=0;i<10;i++)
    {
        num(stuID[i]);
    }
}

void check()
{
    while(1)
    {
        buttonState = digitalRead(pushButton);
        if(!buttonState){ID();}
        else{break;}
    }
}

void loop() {
    showSevenSeg(0,1,1,1,1,1,1); // turn LED A of 7-segment on.
    delay(500);
    check();
    showSevenSeg(1,0,1,1,1,1,1); // turn LED A of 7-segment on.
    delay(500);
    check();
    showSevenSeg(1,1,0,1,1,1,1); // turn LED A of 7-segment on.
    delay(500);
    check();
    showSevenSeg(1,1,1,0,1,1,1); // turn LED A of 7-segment on.
```



```
delay(500);  
check();  
showSevenSeg(1,1,1,1,0,1,1); // turn LED A of 7-segment on.  
delay(500);  
check();  
showSevenSeg(1,1,1,1,1,0,1); // turn LED A of 7-segment on.  
delay(500);  
check();  
}
```

Demo

EXP4

<https://youtu.be/rzM0r-gSWo8>

Reference

- [1] How to Interface a Seven-Segment Display with an Arduino
<https://www.digikey.tw/en/maker/projects/how-to-interface-a-seven-segment-display-with-an-arduino/9c05f147618c4fe3b8bb79acce5c60e3>
- [2] Pull-up resistor, Wikipedia.
https://en.wikipedia.org/wiki/Pull-up_resistor

心得

還沒寫好 QQ